

EN-3212 Electronics

Wheatstone Bridge

Write the symbolic expression for V_a .

Calculate V_a .

Write the symbolic expression for V_b .

Calculate V_b .

Write the symbolic expression for V_{ab} .

Calculate V_{ab} .

