

# EN-3212 Electronics Worksheet 10

## Operational Amplifiers: Signal Conditioning

Draw each operational amplifier circuit. Include resistor values

Components:

Resistors: standard

Op amps: unlimited

Equation:

$$V_{\text{out}} = -0.2V_{\text{in}}$$

Components:

Resistors: standard

Op amps: unlimited

Equation:

$$V_{\text{out}} = 6.1V_{\text{in}}$$

Components:

Resistors: standard

Capacitors: any value

Op amps: unlimited

Equation:

$$V_{\text{out}} = -\frac{1}{0.0013} \int V_{\text{in}} dt$$

# EN-3212 Electronics Worksheet 10

## Operational Amplifiers: Signal Conditioning

Components:

Resistors: standard

Capacitors: any value

Op amps: unlimited

Equation:

$$V_{\text{out}} = -0.00091 \frac{d}{dt} V_{\text{in}}$$

!!Components:

Resistors: standard

Op amps: unlimited

Equation:

$$V_{\text{out}} = \frac{2}{3} V_{\text{in}}$$

!!Components:

Resistors: standard

Op amps: unlimited

Voltage Source: 10volts

Equation:

$$V_{\text{out}} = 2V_1 + -4volts$$

# EN-3212 Electronics Worksheet 10

## Operational Amplifiers: Signal Conditioning

!!Components:

Resistors: standard

Op amps: unlimited

Equation:

$$V_{\text{out}} = 3.3V_1 - \frac{4}{1.5} V_2$$