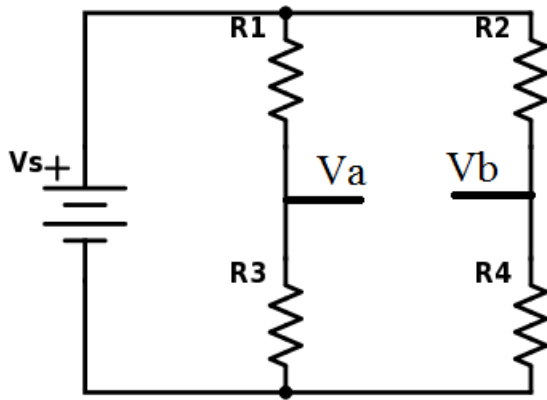


EN-3212 Electronics Worksheet 5

Thevenin's Theorem

The circuit below is called a Wheatstone Bridge. Derive an expression for V_{ab} given the circuit below.



Find V_{ab} if $V_s = 12\text{V}$, $R1 = 1.2\text{k}\Omega$, $R2 = 470\Omega$, $R3 = 500\Omega$, and $R4 = 2\text{k}\Omega$.

EN-3212 Electronics Worksheet 5

Thevenin's Theorem

What would happen if $V_a = V_b$? See what you get when you assume this. Be sure to simplify the expression.

If $V_s = 18\text{V}$, $R_2 = 1\text{k}\Omega$, $R_3 = 3.3\text{k}\Omega$, and $R_4 = 2.4\text{k}\Omega$, what value would R_1 have to be to make $V_{ab} = 0$?

What would happen to V_{ab} if:


R_1 increases?

R_1 decreases?


EN-3212 Electronics Worksheet 5

Thevenin's Theorem

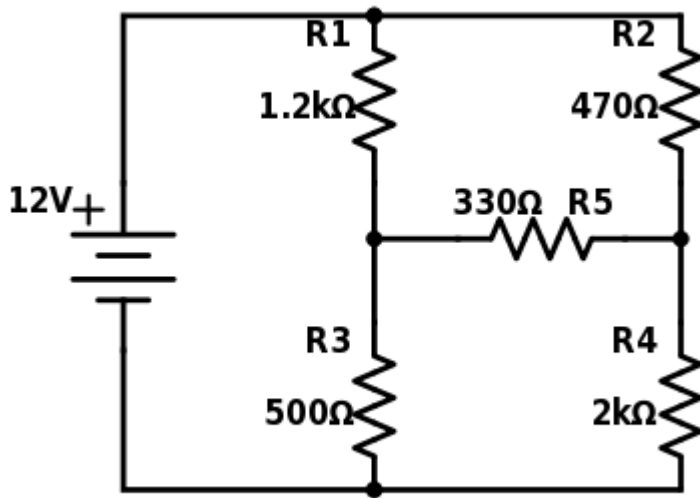Can you find the equivalent resistance of the following circuit? Are any of these resistors in series or in parallel?



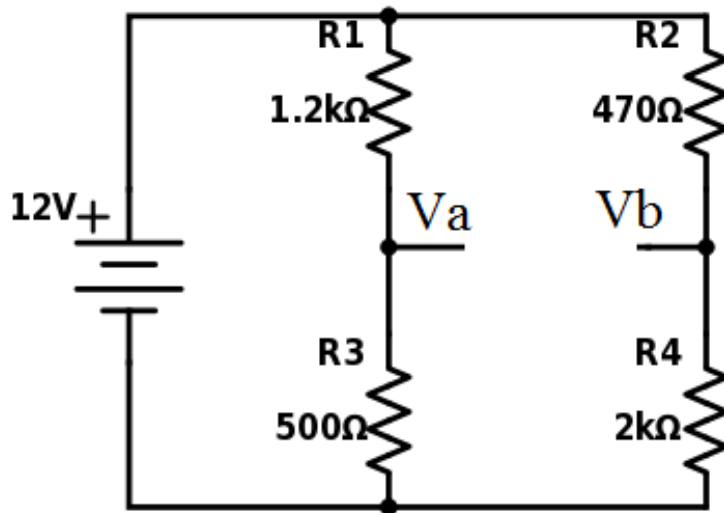Here's what we're going to do. R5 is going to be called our "load resistor". We remove it and leave the two terminals open.




Calculate V_{ab} . This will be the Thevenized voltage.

EN-3212 Electronics Worksheet 5

Thevenin's Theorem

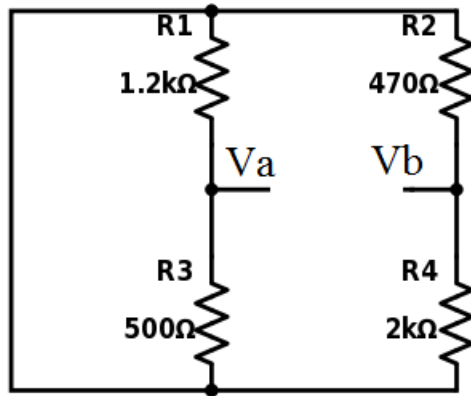
Now, remove V_s and calculate the equivalent resistance between terminals a and b (it may be easier if you redraw this picture). This will be the Thevenized resistance.



EN-3212 Electronics Worksheet 5

Thevenin's Theorem

Now, you can redraw the circuit.

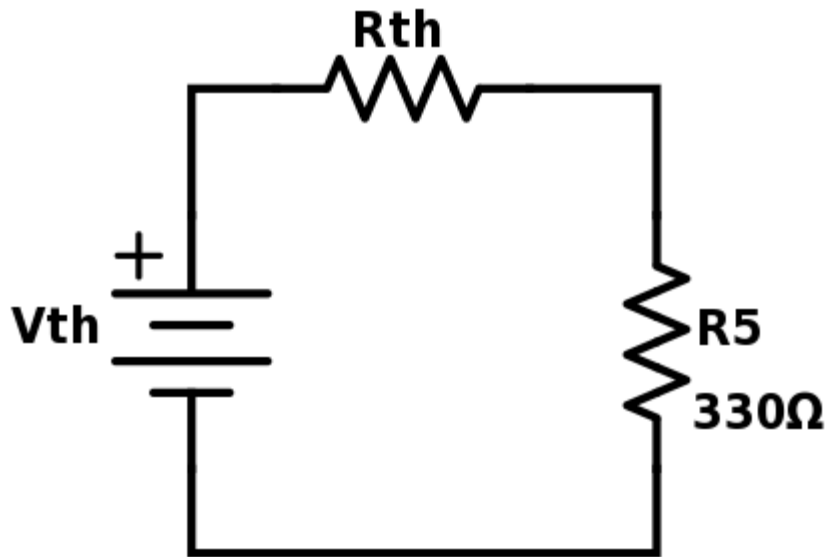


Calculate the current through and voltage drop across $R5$. This will give you the correct value.

EN-3212 Electronics Worksheet 5

Thevenin's Theorem

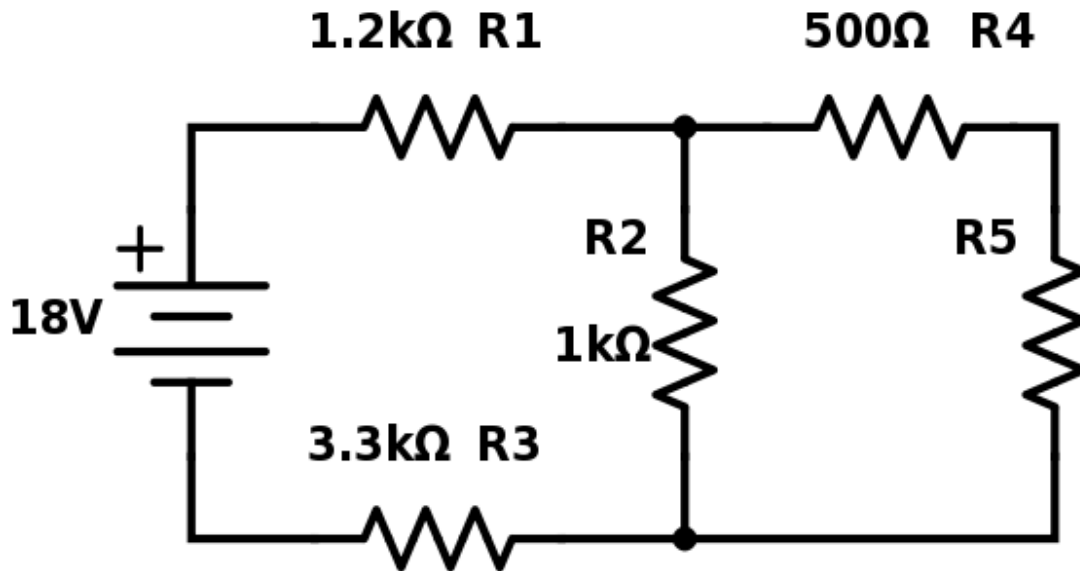Try doing the same of the circuit below for R5. $R5 = 200\Omega$. You can analyze this circuit using the parallel/series method that you know if you would like to verify that your answer is correct.



EN-3212 Electronics Worksheet 5

Thevenin's Theorem

Thevenize the following circuit. Calculate the current through and the voltage drop across R7 if its value 250 Ω .

