

# EN-3212 Electronics Worksheet 8

## Complex Impedance

We will talk about the impedance of elements in an AC circuit as being LIKE resistance in a DC circuit. In some ways, that is a reasonable thing to do. In others it is complete nonsense. At this point, I hope you trust that when I tell you these half-truths it's only to help you reach a complete and more useful conceptual picture of what is going on.

With that in mind, I do want you to think of impedance as being like resistance for this portion of the course. We'll clear up some of the issues with that picture later.

### 1. Resistors:

- a. Draw the schematic symbol for a resistor.
- b. Write an equation relating the resistance of a resistor to its impedance.

### 2. Capacitors:

- a. Draw the schematic symbol for a capacitor.
- b. Write the equation for the capacitive reactance of a capacitor.
- c. Write the equation for the impedance of the capacitor.

### 3. Inductors:

- a. Draw the schematic symbol for an inductor.
- b. Write the equation for the inductive reactance of an inductor.
- c. Write the equation for the impedance of an inductor.

# EN-3212 Electronics Worksheet 8

## Complex Impedance


Answer the following questions given that you are using a 1kHz voltage source.

4. What is the impedance of a  $470\Omega$  resistor?

5. What is the impedance of a  $500\mu\text{f}$  capacitor?

6. What is the impedance of a 20mH inductor?

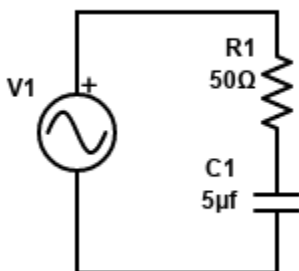
7. Given a 1200 Hz source, find the total impedance of the circuit shown below.




# EN-3212 Electronics Worksheet 8

## Complex Impedance

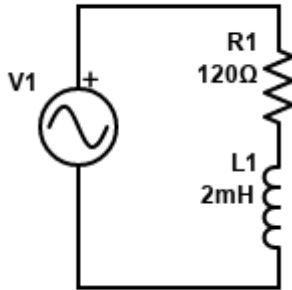
8. Given a 4.1 kHz source, find the total impedance of the circuit shown below.



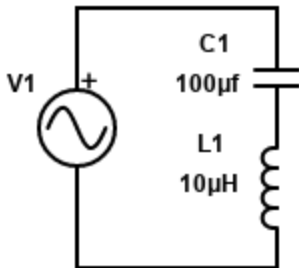9. Given a 100 Hz source, find the total impedance of the circuit shown below.



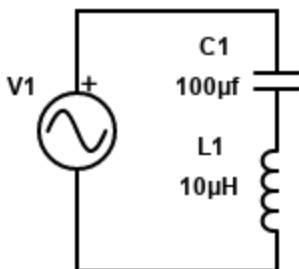
10. Given a 10 kHz source, find the total impedance of the circuit shown below.




# EN-3212 Electronics Worksheet 8

## Complex Impedance

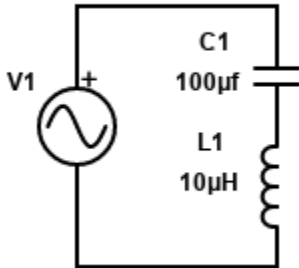
11. Given a 5 kHz source, find the total impedance of the circuit shown below.



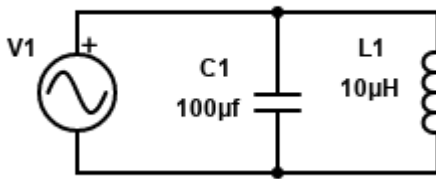
12. Given a 100 Hz source, find the total impedance of the circuit shown below.



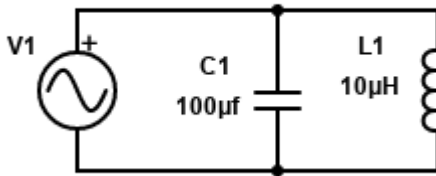13. Given a 10 kHz source, find the total impedance of the circuit shown below.



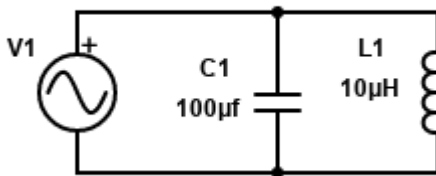
14. Given a 5 kHz source, find the total impedance of the circuit shown below.




# EN-3212 Electronics Worksheet 8

## Complex Impedance

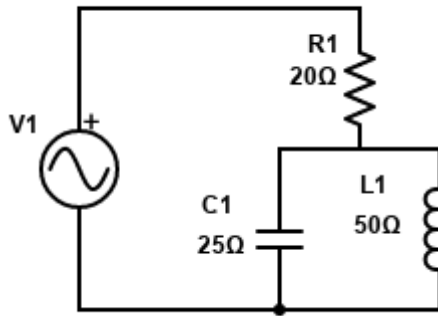
15. Find the total impedance of the circuit shown below.



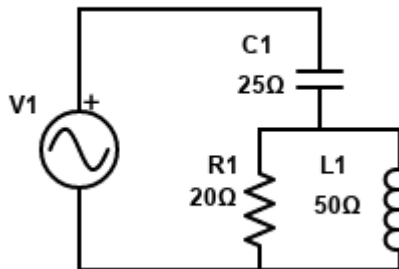16. Find the total impedance of the circuit shown below.



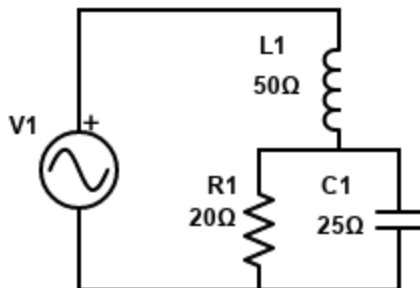17. Find the total impedance of the circuit shown below.



## EN-3212 Electronics Worksheet 8

### Complex Impedance

18. Find the total impedance of the circuit shown below.

